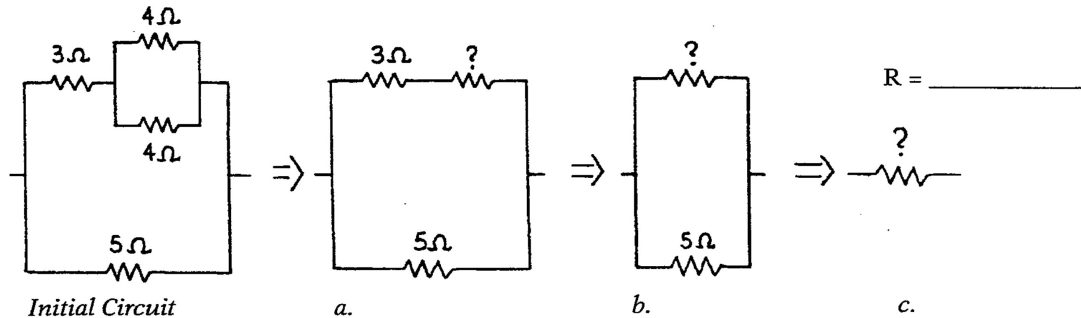


Concept-Development Practice Page
 Chapter 35: Electric Circuits

35-3

Compound Circuits



1. The initial circuit, below left, is a compound circuit made of a combination of resistors. It is reduced to a single equivalent resistance by the three steps, the circuits to its right, *a*, *b*, *c*. In step *a*, show the equivalent resistance of the parallel $4\text{-}\Omega$ resistors. In step *b* combine this in series with the $3\text{-}\Omega$ resistor. In step *c*, combine the last parallel pair to obtain the equivalent resistance of the circuit. (Note the similarity of this circuit and Figure 35-10 in your textbook.)




2. The circuit below is similar to Figure 35-11 in your textbook. In three successive steps, as in Question 1, replace each pair of resistors by a single resistor of equivalent resistance.



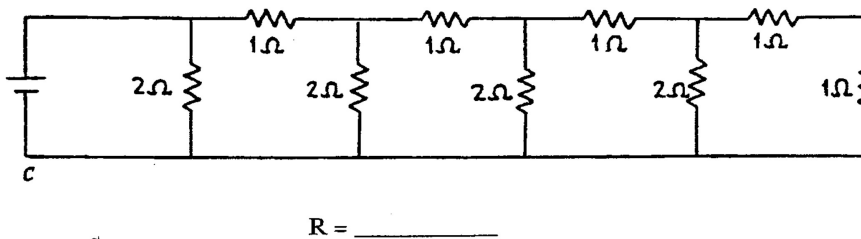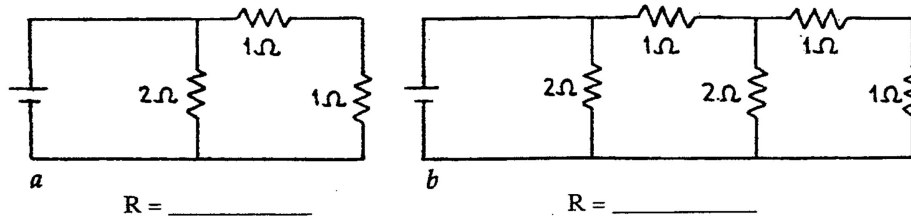
3. Find the equivalent resistance of these three circuits.



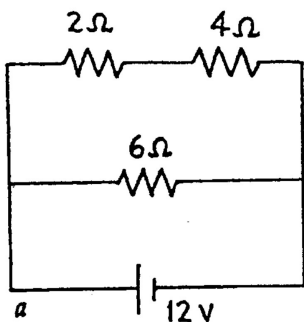
4. The table beside circuit *a* below shows the current through each resistor, the voltage across each resistor, and the power dissipated as heat in each resistor. Find the similar correct values for circuits *b*, *c*, and *d*, and put your answers in the tables shown.




RESISTANCE	CURRENT	VOLTAGE	POWER
2 Ω	2 A	4 V	8 W
4 Ω	2 A	8 V	16 W
6 Ω	2 A	12 V	24 W

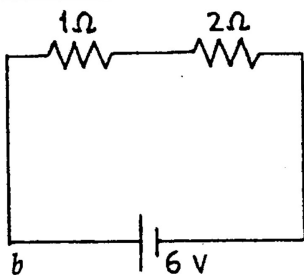

RESISTANCE	CURRENT	VOLTAGE	POWER
1 Ω			
2 Ω			

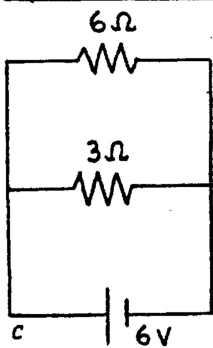

RESISTANCE	CURRENT	VOLTAGE	POWER
6 Ω			
3 Ω			

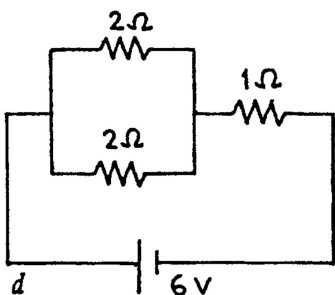

RESISTANCE	CURRENT	VOLTAGE	POWER
2 Ω			
2 Ω			
1 Ω			